

CMOS Matrix-Vector Multiplier

ECE 533 – Final Design Review

Team Members (Group 1):

- Sk Hasibul Alam
- Tanjina Sabrin
- Md Farhan

Outline Review

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix} \cdot \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} ax + by \\ cx + dy \end{bmatrix}$$

Input:

- $a, b, c, d, x, y \rightarrow$ 4-bit unsigned each

Product:

- $ax, by, cx, dy \rightarrow$ 8-bit unsigned each

Output:

- $(ax + by), (cx + dy) \rightarrow$ 9-bit unsigned

What we need:


- 4 × 4 Multiplier
- 8-bit Adder
- Bank of D-Latch

Adder Type:


- Carry-lookahead Adder (CLA)

Where we left: 4-bit CLA unit

Layout

 

Schematic

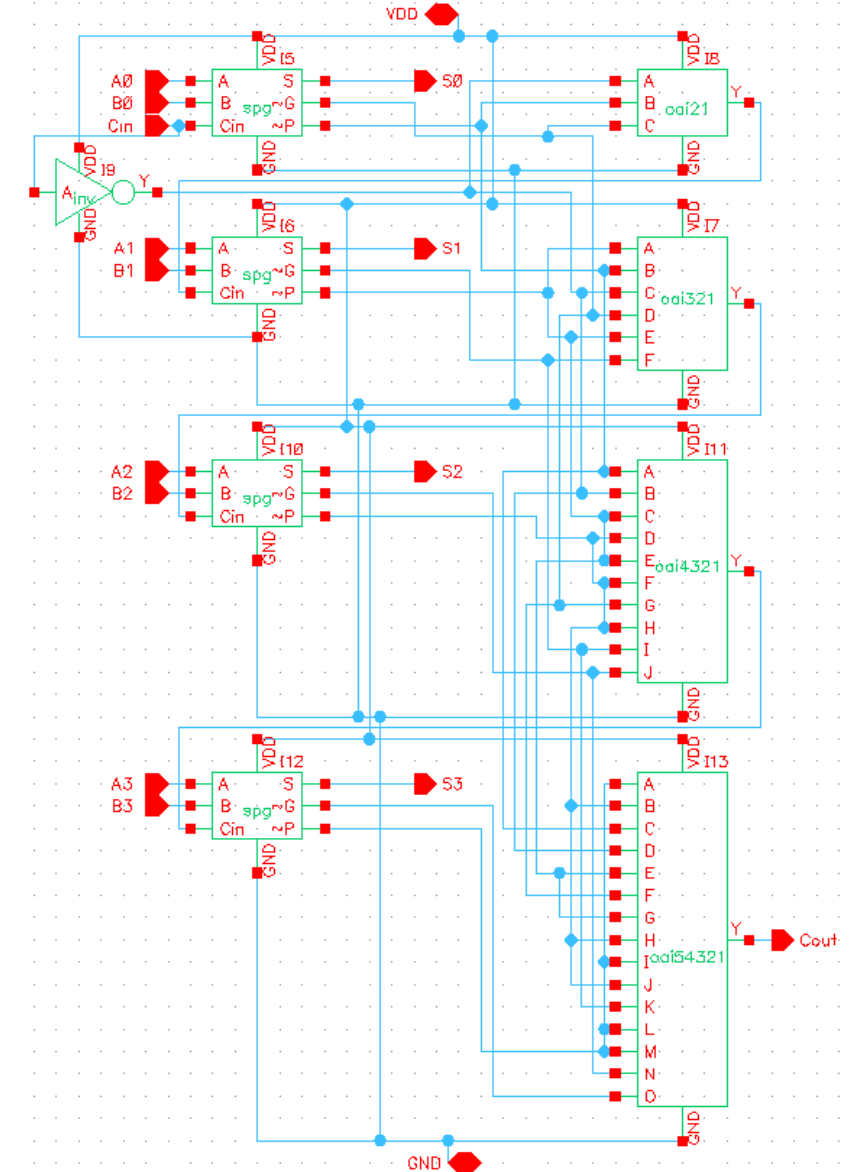

DRC & LVS

```
Running layout DRC analysis
Flat mode
Full checking.
DRC started.....Thu Nov 17 22:34:07 2022
completed ....Thu Nov 17 22:34:07 2022
CPU TIME = 00:00:00 TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "fa_test layout" *****
Total errors found: 0
```

```
Net-list summary for /home/salam12/ece533/cadence/LVS/layout/netlist
count
78 nets
16 terminals
67 pmos
67 nmos


Net-list summary for /home/salam12/ece533/cadence/LVS/schematic/netlist
count
78 nets
16 terminals
67 pmos
67 nmos
```

```
Terminal correspondence points
N68 N3 A0
N67 N6 A1
N66 N11 A2
N65 N26 A3
N76 N2 N0
N75 N5 B1
N74 N24 B2
N72 N27 B3
N70 N4 Cin
N71 N15 Cout
N69 N1 GND
N64 N9 S0
N63 N10 S1
N62 N13 S2
N77 N25 S3
N73 N0 VDD
```

Devices in the netlist but not in the files:
pmos nmos

The net-lists match.

4x4 Multiplier

 


Things to consider:

- We need
 - 5 units of CLA4
 - 16 units of AND2.
- C_{out} of last CLA4 is unnecessary.
 - Remove OAI54321 (30 T) from that.
- P7 will be slowest (obviously).

continued...

Layout

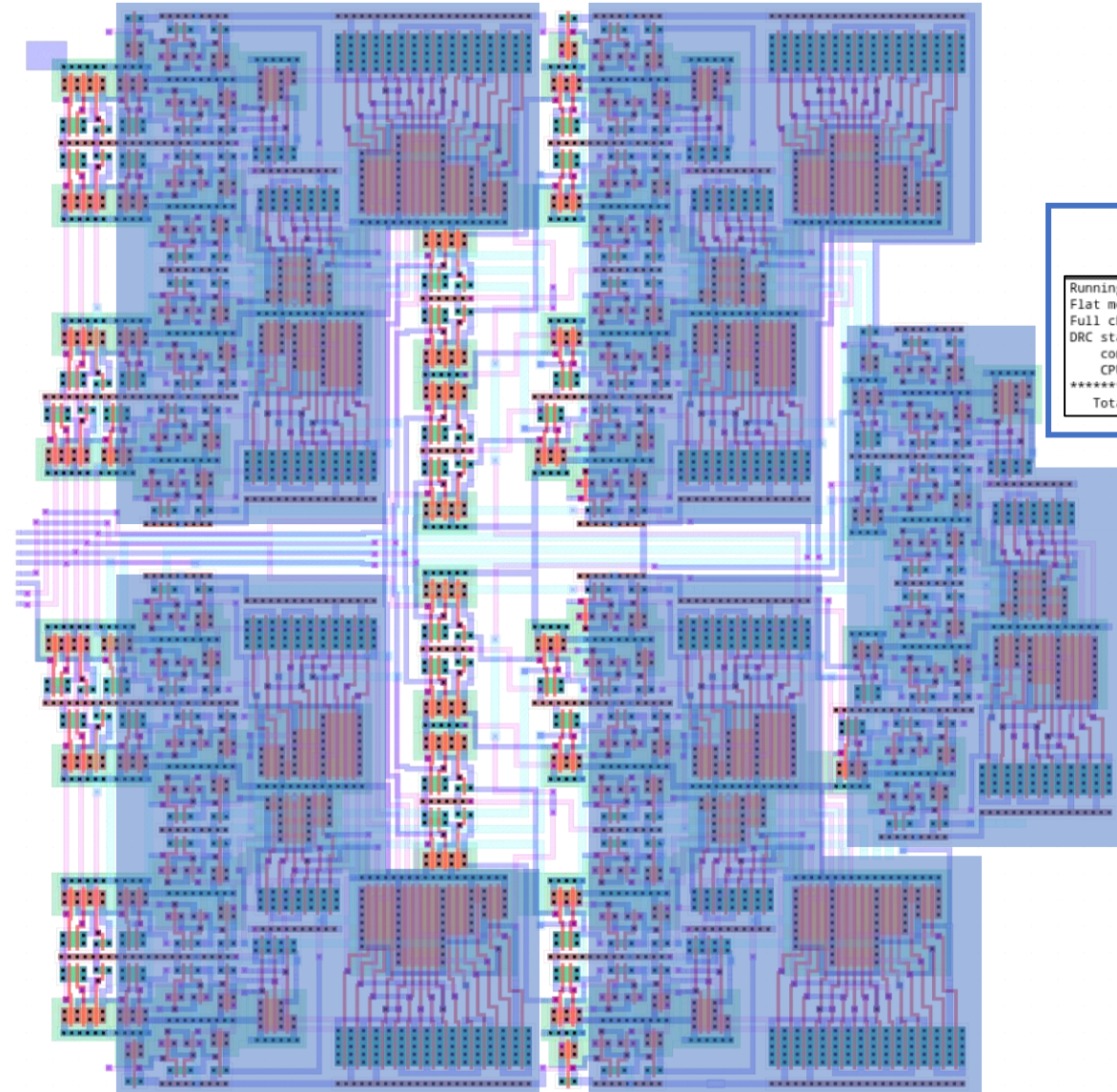

DRC & LVS

```
Running layout DRC analysis
Flat mode
Full checking.
DRC started.....Thu Dec 1 22:38:49 2022
completed ....Thu Dec 1 22:38:50 2022
CPU TIME = 00:00:00 TOTAL TIME = 00:00:01
***** Summary of rule violations for cell "multi4 layout" *****
Total errors found: 0
```

```
Net-list summary for /home/salam12/ece533/cadence/LVS/layout/netlist
count
378 nets
18 terminals
368 pmos
368 nmos

Net-list summary for /home/salam12/ece533/cadence/LVS/schematic/netlist
count
378 nets
18 terminals
368 pmos
368 nmos
```


Terminal correspondence points

N363	N3	A0
N362	N2	A1
N361	N1	A2
N360	N0	A3
N377	N49	B0
N376	N48	B1
N375	N47	B2
N373	N46	B3
N364	N12	GND
N372	N44	P0
N371	N40	P1
N370	N35	P2
N369	N33	P3
N368	N32	P4
N367	N43	P5
N366	N45	P6
N365	N34	P7
N374	N18	VDD

Devices in the netlist but not in the rules:
pmos nmos


The net-lists match.

Schematic

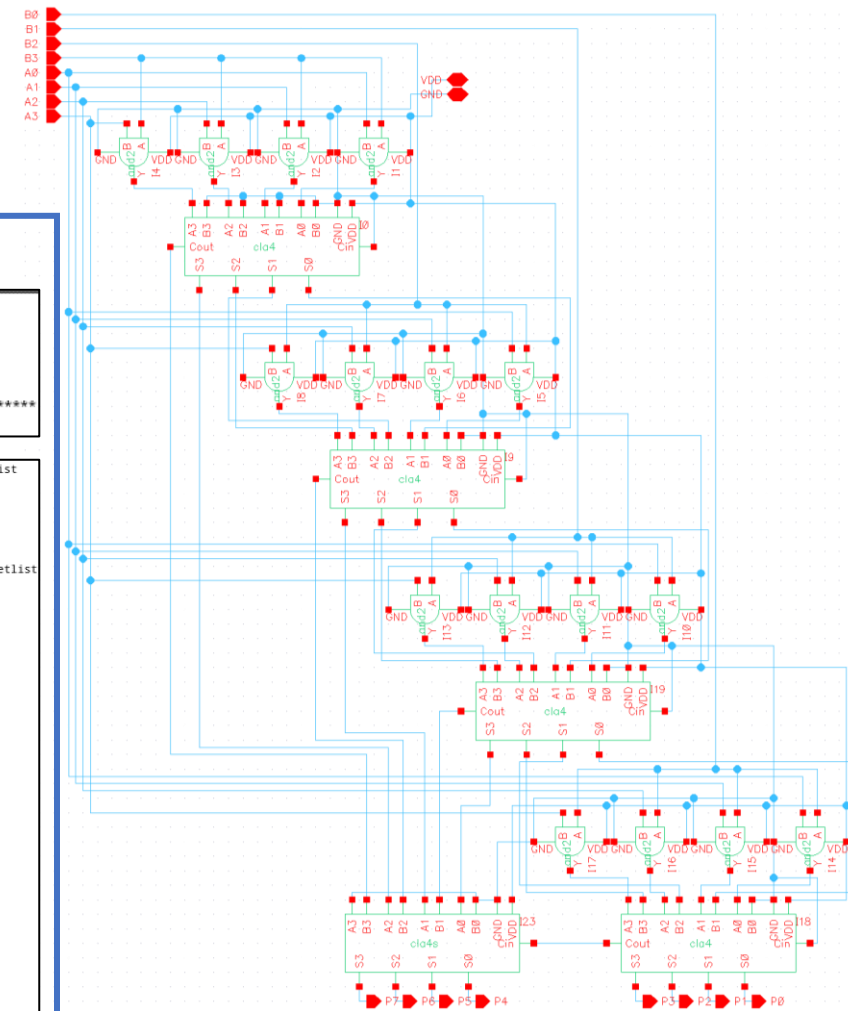


continued...

 4x4 Multiplier Transient Analysis (cropped)



Schematic

 


Extracted

Transistor Count			
Module	#Unit	FET/unit	Total FET
CLA4	5	134	670
AND2	16	6	96
OAI54321*	-1	30	-30
Aggregate Count			736

* We don't need C_{out} of last CLA4.

continued...

 


Note:

- Inputs are changing at 25 MHz here.
 - could be increased up to 50 MHz
- t_{pd} is 8 ns → will affect next stage


Dynamic D-Latch

Transmission Gate based

 

- ✓ Slightly faster:
 - Both FETs work in parallel

Clocked CMOS (C²MOS)

 


- ✓ Slightly smaller:
 - Eliminates 2 contacts

Problem with dynamic output:


- May lose value due to subthreshold leakage
- May lose value during burn-in test

continued...


Schematic

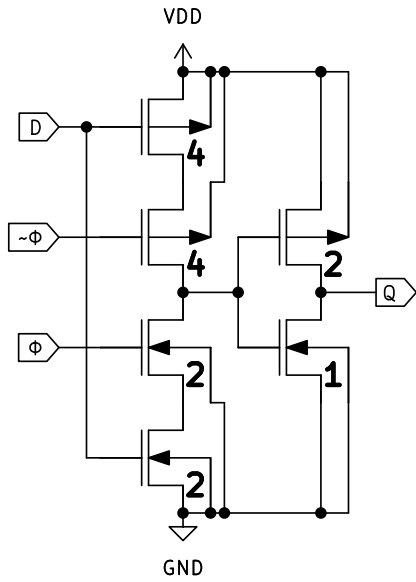

Layout

 

 C²MOS Latch Transient Analysis (extracted)




As expected,

- Q follows D while clk is true.
- Q holds Q_{old} while clk is false.

But,

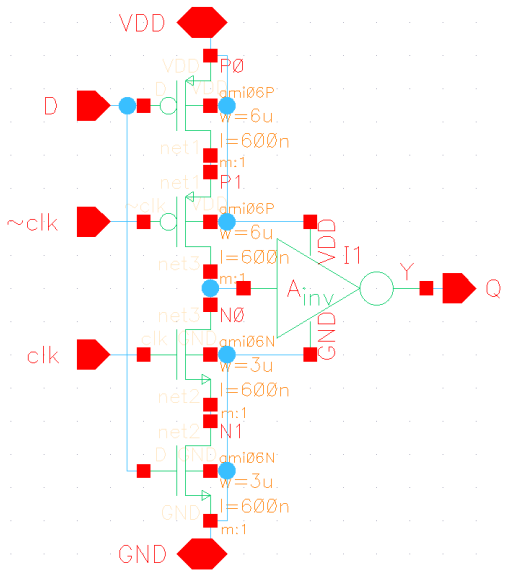
- t_{pdq} is not bad, but not good either.




Possible Methods of Final Design

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix} \cdot \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} ax + by \\ cx + dy \end{bmatrix}$$

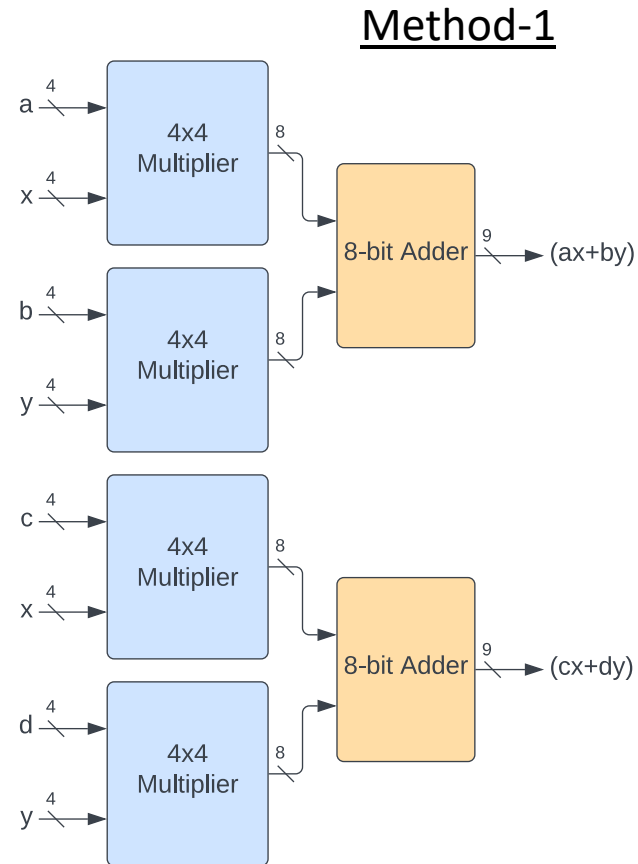Assume:
Inputs are driven from D-FF.
Outputs are sampled by D-FF.



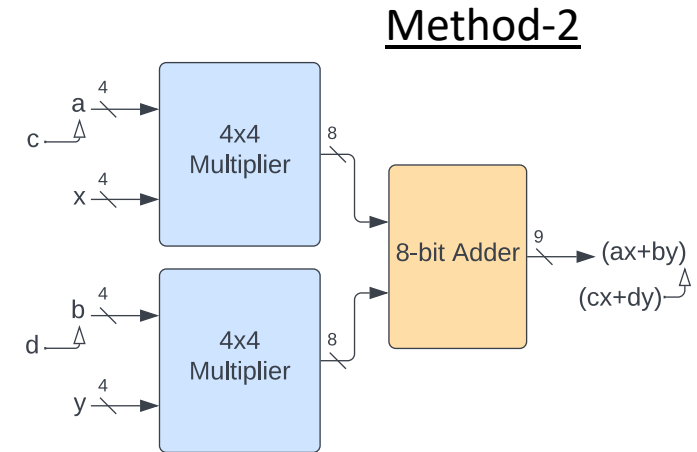- ✓ Fastest method (T_{clk})
 - Both outputs concurrently available after t_{pd}
 - Outputs ready to be sampled at next posedge of D-FF
- ✓ No internal clock needed
- ❖ Enormous area required




- ❖ Moderately fast method ($2 \times T_{clk}$)
 - Inputs are serially driven.
 - 2nd output ($cx + dy$) is sampled one T_{clk} after 1st output is sampled.
- ✓ No internal clock needed
- ❖ Huge area still required
 - even after 50% reduction

	Posedge		
	0	1	2
In1	a	c	
In2	x	x	
In3	b	d	
In4	y	y	
Out		$ax + by$	$cx + dy$

continued...


Method-3

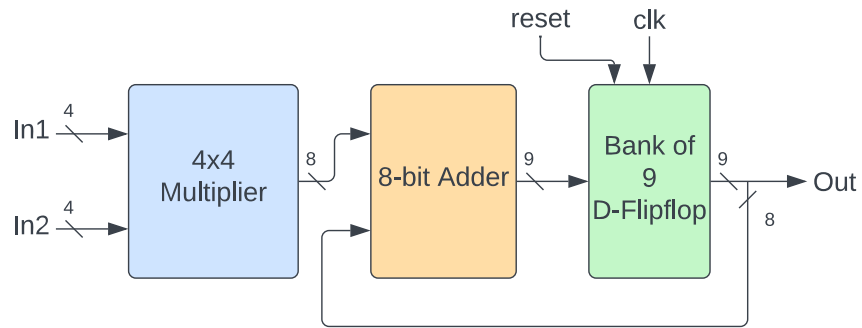

- ❖ Slowest method ($4 \times T_{clk}$)
 - Inputs are serially driven.
- ❖ Internal clock needed
- ❖ Reset signal needed
 - Reset the D-FF bank at beginning, reset it again after $(ax + by)$ is sampled.
- ✓ Small area required

	Posedge				
	0	1	2	3	4
In1	a	b	c	d	
In2	x	y	x	y	
Out		$ax + 0$	$ax + by$	$cx + 0$	$cx + dy$

Method-4

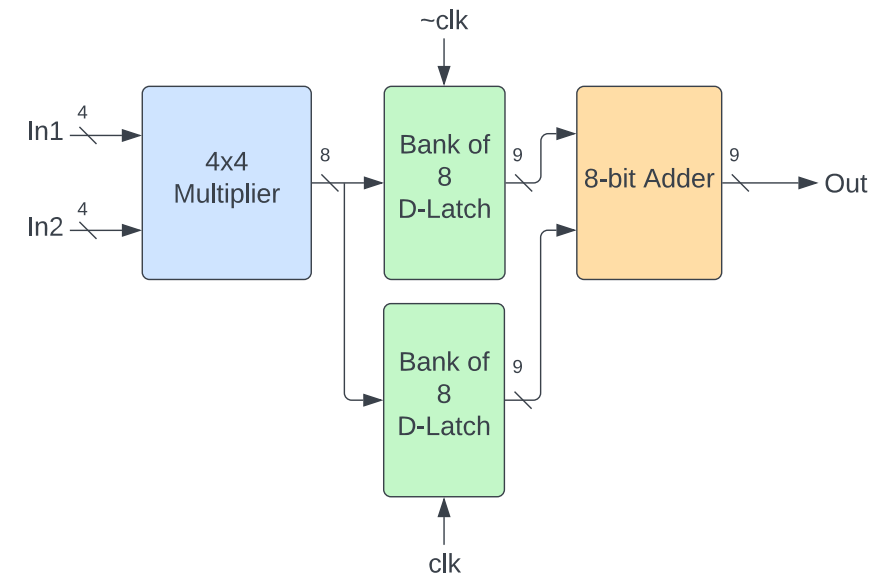


- ✓ Moderately fast method ($2 \times T_{clk}$)
 - TDM is employed for D-Latch banks.
- ❖ Internal clock needed
- ✓ Reset signal not needed
- ✓ Smallest area required


	clk Level			
	1	0	1	0
In1	a	b	c	d
In2	x	y	x	y
Out	$ax + ?$	$ax + by$	$cx + by$	$cx + dy$

Full Design: Matrix-Vector Multiplier

Layout

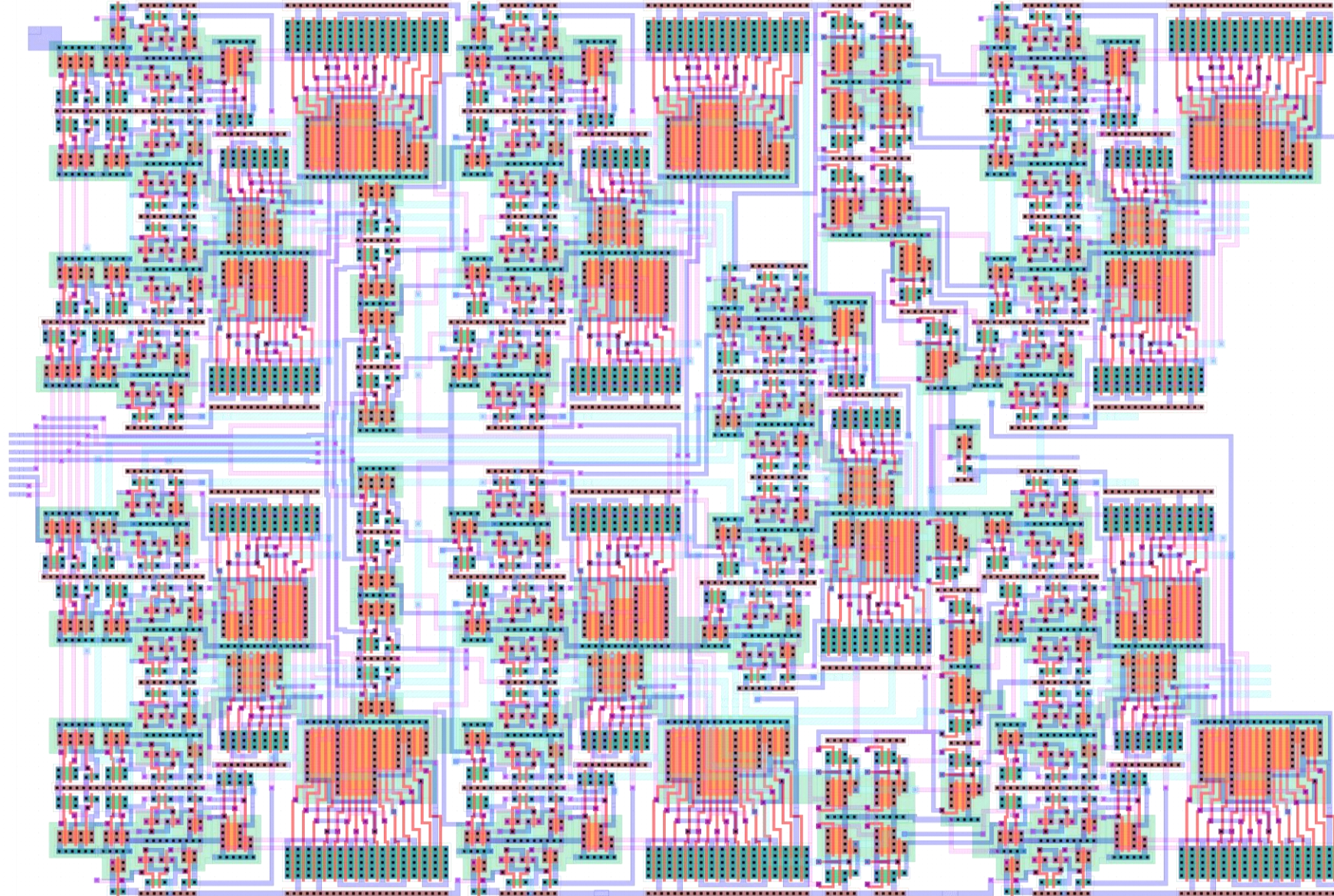

Schematic

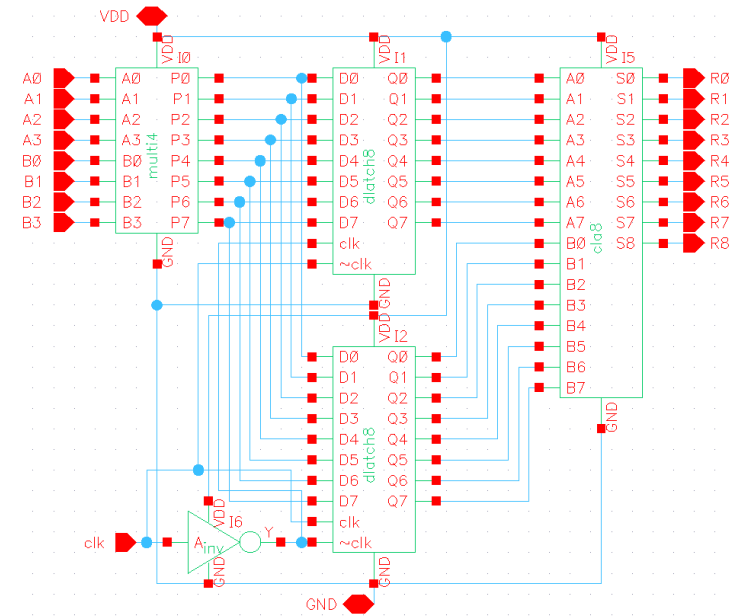

```
Net-list summary for /home/salam12/ece533/cadence/LVS/layout/netlist
count
578 nets
20 terminals
551 pmos
551 nmos

Net-list summary for /home/salam12/ece533/cadence/LVS/schematic/netlist
count
578 nets
20 terminals
551 pmos
551 nmos

Terminal correspondence points
N564 N14 A0
N562 N15 A1
N560 N35 A2
N558 N36 A3
N577 N37 B0
N576 N38 B1
N575 N39 B2
N573 N40 B3
N571 N17 GND
N570 N41 R0
N569 N42 R1
N568 N43 R2
N567 N0 R3
N566 N1 R4
N565 N2 R5
N563 N3 R6
N561 N4 R7
N559 N5 R8
N574 N16 VDD
N572 N44 clk

Devices in the netlist but not in the rules:
pmos nmos

The net-lists match.
```

DRC




```
Running layout DRC analysis
Flat mode
Full checking.
DRC started.....Mon Dec 5 17:29:17 2022
completed ...Mon Dec 5 17:29:18 2022
CPU TIME = 00:00:00 TOTAL TIME = 00:00:01
***** Summary of rule violations for cell "matvec layout"
Total errors found: 0
```

LVS




continued...

Transient Analysis

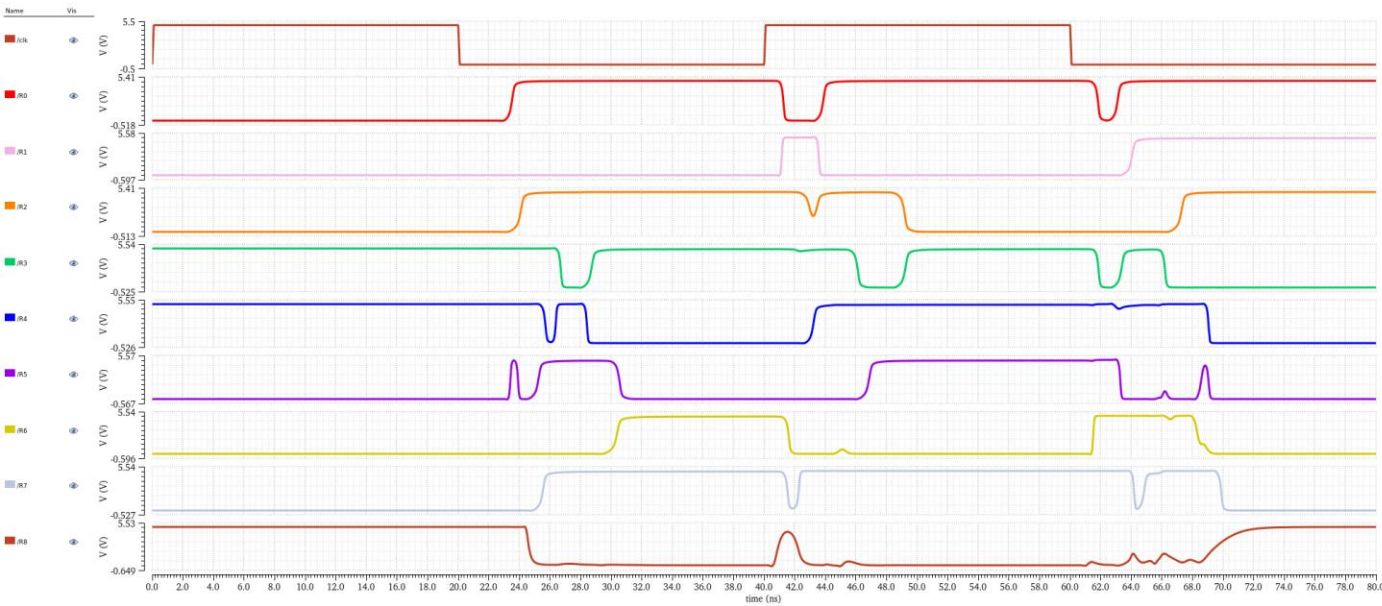

Schematic


Transistor Count			
Module	#Unit	FET/unit	Total FET
Multiplier	1	736	736
D-Latch	16	6	96
CLA4	2	134	268
INV2	1	2	2
Aggregate Count			1102

 

Extracted

$$\begin{aligned} \text{Total Area} &= 297.75 \mu\text{m} \times 204 \mu\text{m} \\ &= 0.0607 \text{ mm}^2 \end{aligned}$$

continued...

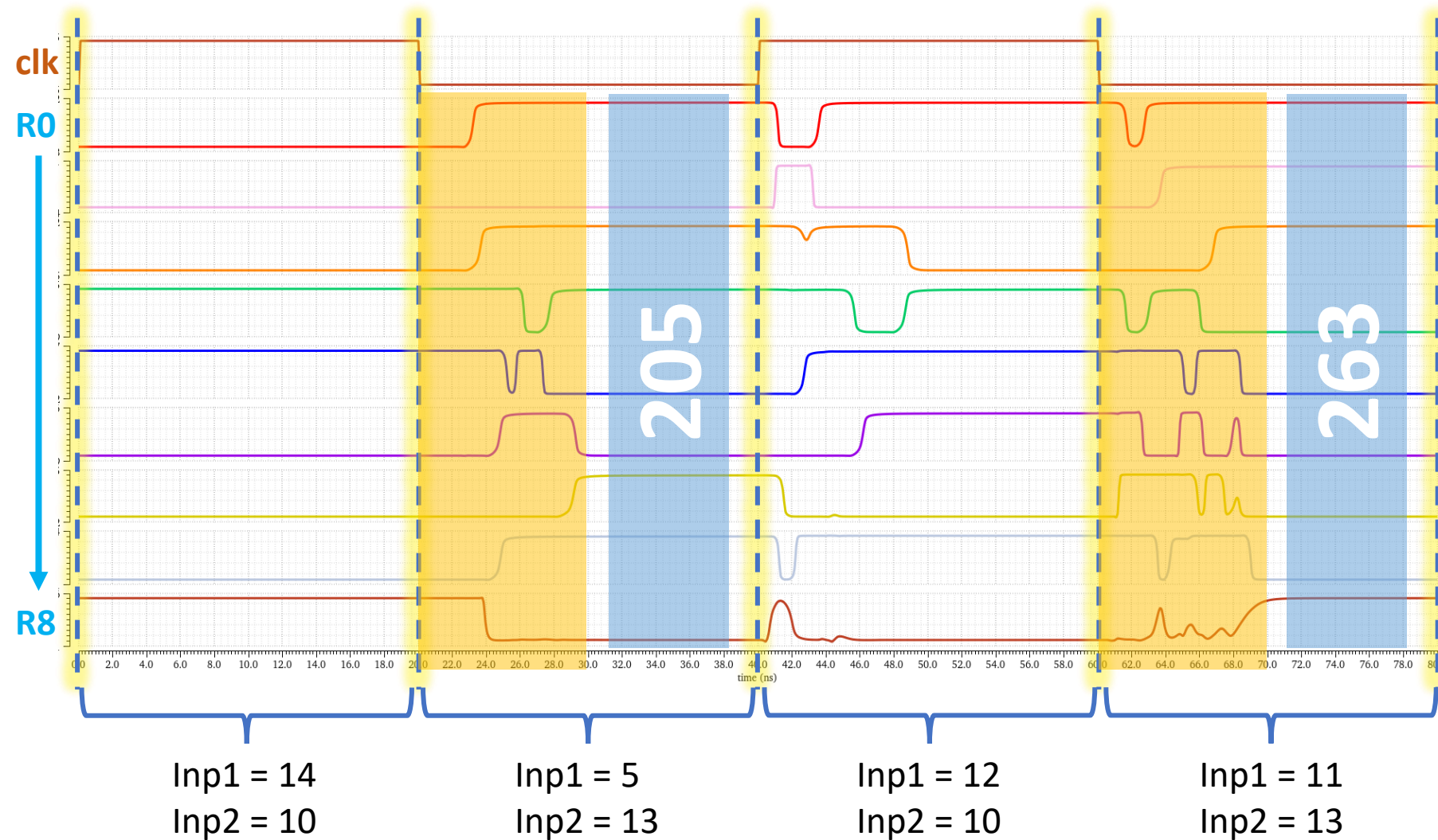

□ Test Case:

$$\begin{bmatrix} 14 & 5 \\ 12 & 11 \end{bmatrix} \cdot \begin{bmatrix} 10 \\ 13 \end{bmatrix} = \begin{bmatrix} 205 \\ 263 \end{bmatrix}$$

■ 205 = b0_1100_1101

■ 263 = b1_0000_0111

Note:

- `clk` frequency is 25 MHz here.
 - can be increased up to 45 MHz
- t_{pd} is 9 ns.

Conclusion

Problems we faced

- Only up to M3 was available.
- Too much emphasis upon equal R_{rise} & R_{fall}
- D-FF or D-Latch?
- Placement of last CLA after D-Latch
- OAI54321: Height vs. Width

Problems in our design

- 4x4 Multiplier
 - Unnecessary \overline{P} , \overline{G} from last CLA4
 - Unnecessary XNOR2 gates at peripheral
- Final design
 - Not running at 80 MHz as predicted

Questions?
Concerns?
Comments?