

CMOS Matrix-Vector Multiplier

ECE 533 – Project Design Review

Team Members (Group 1):

- Sk Hasibul Alam
- Tanjina Sabrin
- Md Farhan

Brief Outline

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix} \cdot \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} ax + by \\ cx + dy \end{bmatrix}$$

Input:

- $a, b, c, d, x, y \rightarrow$ 4-bit unsigned each

Product:

- $ax, by, cx, dy \rightarrow$ 8-bit unsigned each

Output:

- $(ax + by), (cx + dy) \rightarrow$ 9-bit unsigned




What we need:

- 4×4 Multiplier
- 8-bit Adder
- Banks of D-Latch




Adder Type:

- Carry-lookahead Adder (CLA)

4x4 Unsigned Multiplier

   

continued...

   

Propagate & Generate (PG) Logic

A	B	C _{in}	C _{out}	S	P	G
0	0	0	0	0	0	0
		1	0	1		
0	1	0	0	1	1	0
		1	1	0		
1	0	0	0	1	1	0
		1	1	0		
1	1	0	1	0	0	1
		1	1	1		

Propagate:

- C_{out} is true if C_{in} is true.
P = A ⊕ B

Generate:

- C_{out} is true.
G = A · B

$$S = (A \oplus B) \oplus C_{in} = P \oplus C_{in}$$

$$C_{out} = G + P \cdot C_{in}$$

continued...

- Generalized formula:

$$C_{i+1} = G_i + P_i \cdot C_i$$

- For 4-bit CLA unit:

$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot C_1$$

$$= G_1 + G_0 \cdot P_1 + C_0 \cdot P_0 \cdot P_1$$

$$C_3 = G_2 + P_2 \cdot C_2$$

$$= G_2 + G_1 \cdot P_2 + G_0 \cdot P_1 \cdot P_2 + C_0 \cdot P_0 \cdot P_1 \cdot P_2$$

$$C_4 = G_3 + P_3 \cdot C_3$$


$$= G_3 + G_2 \cdot P_3 + G_1 \cdot P_2 \cdot P_3 + G_0 \cdot P_1 \cdot P_2 \cdot P_3 + C_0 \cdot P_0 \cdot P_1 \cdot P_2 \cdot P_3$$

Remember:

$$P_i = A_i \oplus B_i$$

$$G_i = A_i \cdot B_i$$




4-bit CLA unit (*unoptimized*)

 

Transistor Count			
Gate	#Unit	FET/unit	Total FET
XOR2	8	6	48
AND2	8	6	48
AND3	3	8	24
AND4	2	10	20
AND5	1	12	12
OR2	1	6	6
OR3	1	8	8
OR4	1	10	10
OR5	1	12	12
Aggregate Count			188

Note: *Inputs are unavailable in complemented form.*

Road to Optimization

   


Transistor Count			
Gate	#Unit	FET/unit	Total FET
XOR2	2	6	12
AND2	1	6	6
Aggregate Count			18


Transistor Count			
Gate	#Unit	FET/unit	Total FET
XNOR2	2	6	12
NAND2	1	4	4
Aggregate Count			16

continued...


XOR2 Designs

 


16 T

 


12 T

 


12 T

 


12 T

 

10 T

 


4 T

 


6 T

continued...

 


Ref: J. Wang, S. Fang, and W. Feng, "New efficient designs for XOR and XNOR functions on the transistor level," in *IEEE Journal of Solid-State Circuits*, vol. 29, no. 7, pp. 780-786, July 1994, doi: 10.1109/4.303715.


XNOR2 Layout

 

XNOR2 Schematic

 


XNOR2 Transient Analysis

 


continued...


NAND2 Schematic

 

NAND2 Stick Diagram


 


NAND2 Layout

 


continued...

SPG unit Schematic

  


NAND2

SPG unit Layout

 

continued...

SPG unit Transient Analysis

 

Observation:



- S is slowest, \overline{G} is fastest.
- \overline{P} , \overline{G} can be directly used for next PG blocks instead of P , G . (But how?)

PG Logic: 1st Stage


$$C_1 = G_0 + P_0 \cdot C_0$$

$$= \overline{\overline{G_0 + P_0 \cdot C_0}}$$
  
$$= \overline{\overline{G_0} \cdot (\overline{P_0} + \overline{C_0})} \rightarrow \text{OAI21}$$




6T instead of 12T

 


continued...


OAI21 Schematic

 



OAI21 Stick Diagram

 

OAI21 Layout


 


OAI21 Transient Analysis

  


PG Logic: 2nd Stage
  
$$\begin{aligned}
 C_2 &= G_1 + G_0 \cdot P_1 + C_0 \cdot P_0 \cdot P_1 \\
 &= \overline{\overline{G_1 + G_0 \cdot P_1 + C_0 \cdot P_0 \cdot P_1}} \\
 &= \overline{\overline{G_1} \cdot (\overline{G_0 + P_1}) \cdot (\overline{C_0 + P_0 + P_1})} \\
 &\quad \hookrightarrow \text{OAI321}
 \end{aligned}$$




↓ 12T instead of 22T

 


continued...


OAI321 Schematic

 



OAI321 Stick Diagram

 

OAI321 Layout

 

OAI321 Transient Analysis

 
 


PG Logic: 3rd Stage


$$C_3 = G_2 + G_1 \cdot P_2 + G_0 \cdot P_1 \cdot P_2 + C_0 \cdot P_0 \cdot P_1 \cdot P_2$$

$$= \overline{G_2} \cdot (\overline{G_1} + \overline{P_2}) \cdot (\overline{G_0} + \overline{P_1} + \overline{P_2}) \cdot (\overline{C_0} + \overline{P_0} + \overline{P_1} + \overline{P_2})$$

↪ OAI4321

  


↓ 20T instead of 34T

 


continued...


OAI4321 Schematic

 



OAI4321 Stick Diagram

 

OAI4321 Layout

 

OAI4321 Transient Analysis (cropped)

 
 


PG Logic: 4th Stage


$$C_4 = G_3 + G_2 \cdot P_3 + G_1 \cdot P_2 \cdot P_3 + G_0 \cdot P_1 \cdot P_2 \cdot P_3 + C_0 \cdot P_0 \cdot P_1 \cdot P_2 \cdot P_3$$

$$= \overline{G_3} \cdot (\overline{G_2} + \overline{P_3}) \cdot (\overline{G_1} + \overline{P_2} + \overline{P_3}) \cdot (\overline{G_0} + \overline{P_1} + \overline{P_2} + \overline{P_3}) \cdot (\overline{C_0} + \overline{P_0} + \overline{P_1} + \overline{P_2} + \overline{P_3})$$

↪ OAI54321

  


30T instead of 48T

 


continued...


OAI54321 Schematic

 



OAI54321 Stick Diagram

 

OAI54321 Layout

 


OAI54321 Transient Analysis (cropped)

  


4-bit CLA unit

Layout

 

Schematic

 

DRC & LVS

Running layout DRC analysis
Flat mode
Full checking.
DRC started.....Thu Nov 17 22:34:07 2022
completedThu Nov 17 22:34:07 2022
CPU TIME = 00:00:00 TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "fa_test layout" *****
Total errors found: 0

Net-list summary for /home/salam12/ece533/cadence/LVS/layout/netlist
count
78 nets
16 terminals
67 pmos
67 nmos


Net-list summary for /home/salam12/ece533/cadence/LVS/schematic/netlist
count
78 nets
16 terminals
67 pmos
67 nmos

Terminal correspondence points
N68 N3 A0
N67 N6 A1
N66 N11 A2
N65 N26 A3
N76 N2 B0
N75 N5 B1
N74 N24 B2
N72 N27 B3
N70 N4 Cin
N71 N15 Cout
N69 N1 GND
N64 N9 S0
N63 N10 S1
N62 N13 S2
N77 N25 S3
N73 N0 VDD


Devices in the netlist but not in the rules:
pmos nmos
The net-lists match.

continued...

CLA4 Transient Analysis (*cropped*)

 

Schematic

 

Extracted

Transistor Count			
Gate	#Unit	FET/unit	Total FET
SPG	4	16	64
INV	1	2	2
OAI21	1	6	6
OAI321	1	12	12
OAI4321	1	20	20
OAI54321	1	30	30
Aggregate Count			134

instead of **188**

Project Progress

Completed

- CLA4 unit
 - Layout & Schematic
 - NAND2
 - INV
 - XNOR2
 - OAI_s

Remaining

- 4 × 4 Multiplier
 - #CLA4 unit needed → 5
 - #AND2 unit needed → 16
- 8-bit Adder
 - #CLA4 unit needed → 2
- Bank of D-Latches

Questions?
Concerns?
Comments?