

Direct Memory Access Controller

Design Review

ECE 551 – SoC Design

Members (Team 4):

- Sk Hasibul Alam
- Milad Tanavardi Nasab
- Tanjina Sabrin

What is Direct Memory Access?


Feature that enables some hardware subsystems to access primary memory independent from the CPU.

From the CPU's perspective, it:

initiates the transfer first

does other tasks while the transfer is ongoing

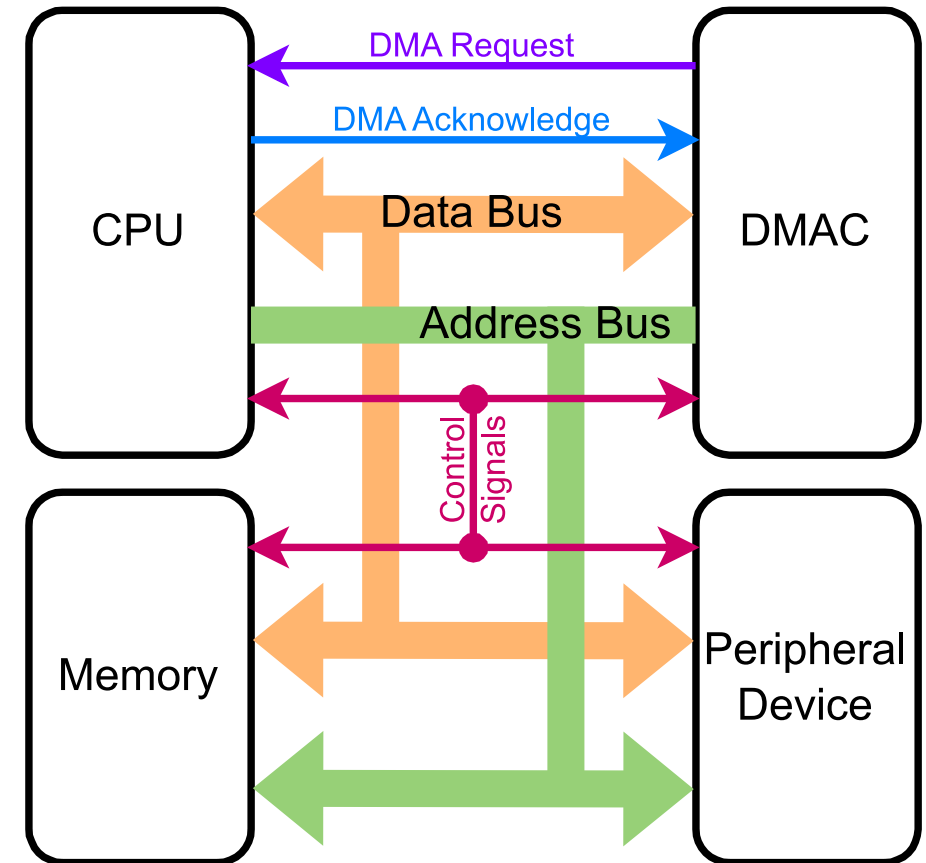waits for the DMAC to interrupt it when the operation is complete





System with AXI4-Lite

AXI = **A**dvanced **eX**tensible **I**nterface


Communicates using 5 independent channel sets:

- Read Address channel (AR)
- Read Data channel (R)
- Write Address channel (AW)
- Write Data channel (W)
- Write Response channel (B)

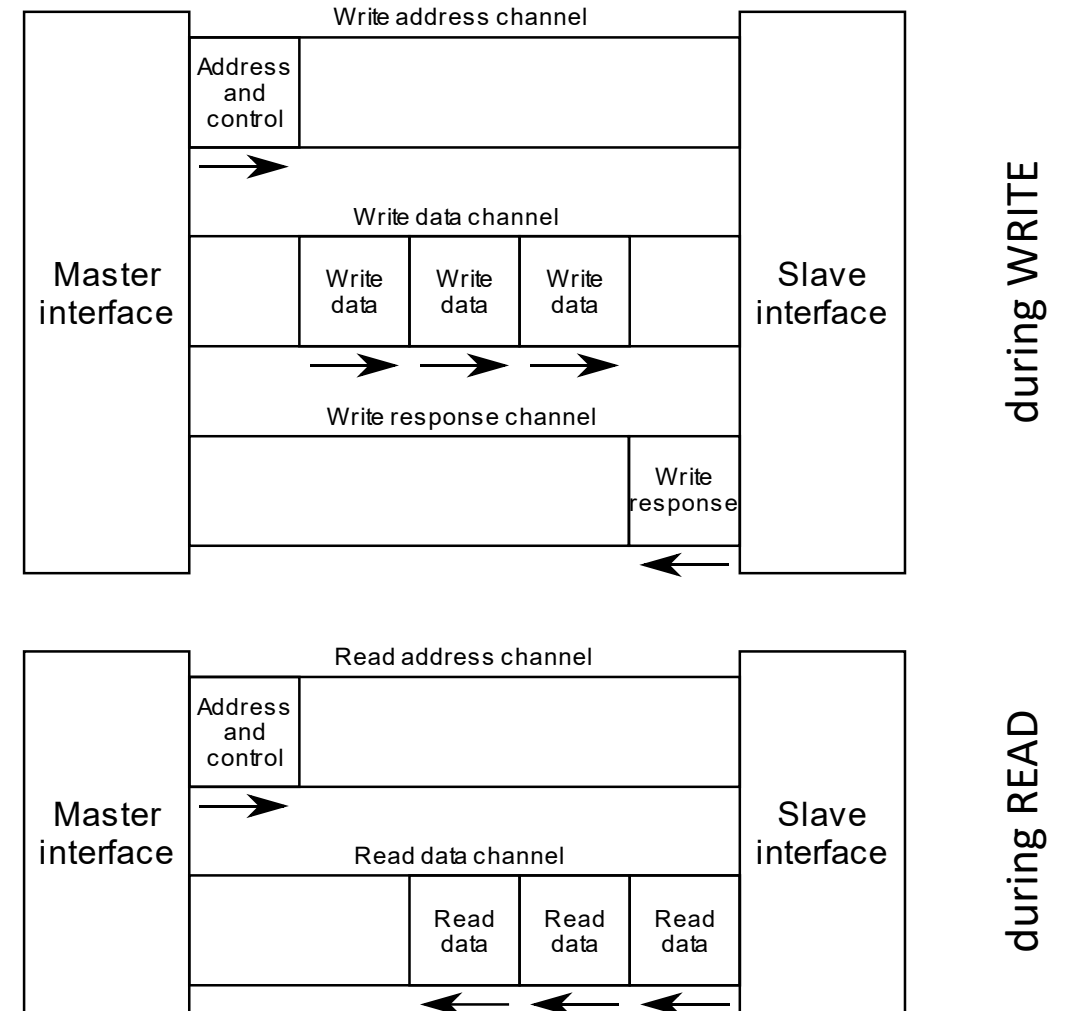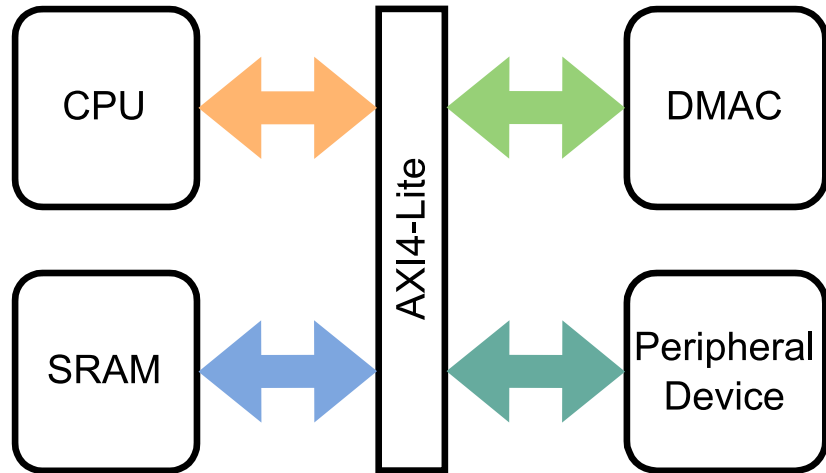


AXI4-Lite Transaction



Read Cycle

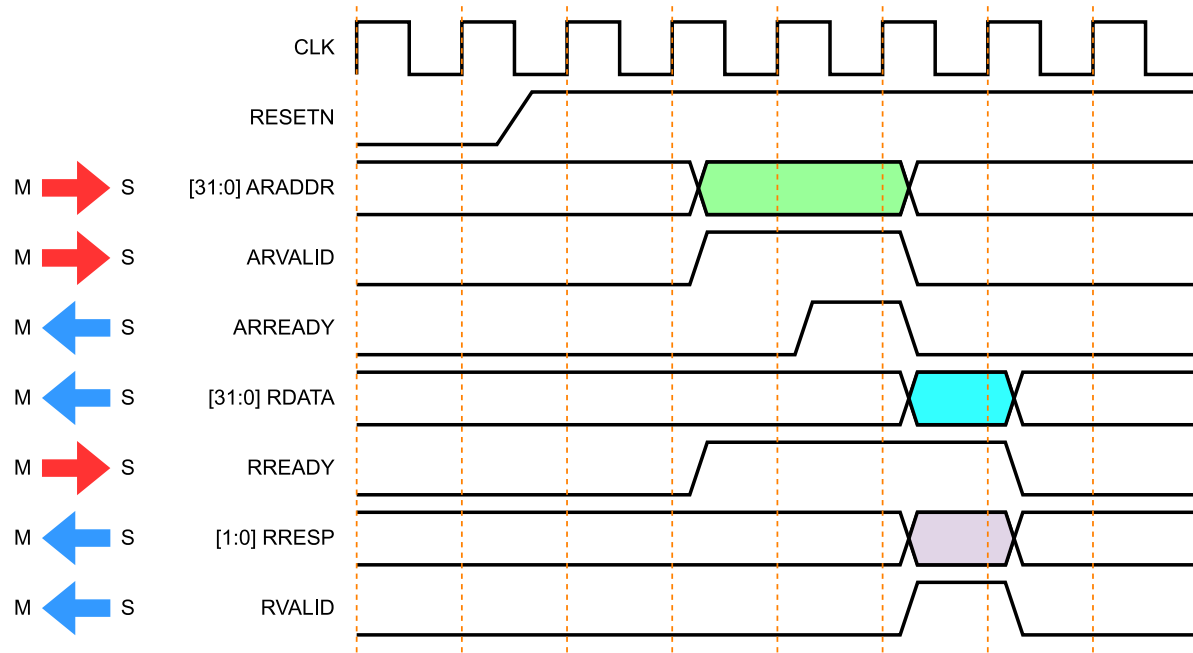



Write Cycle

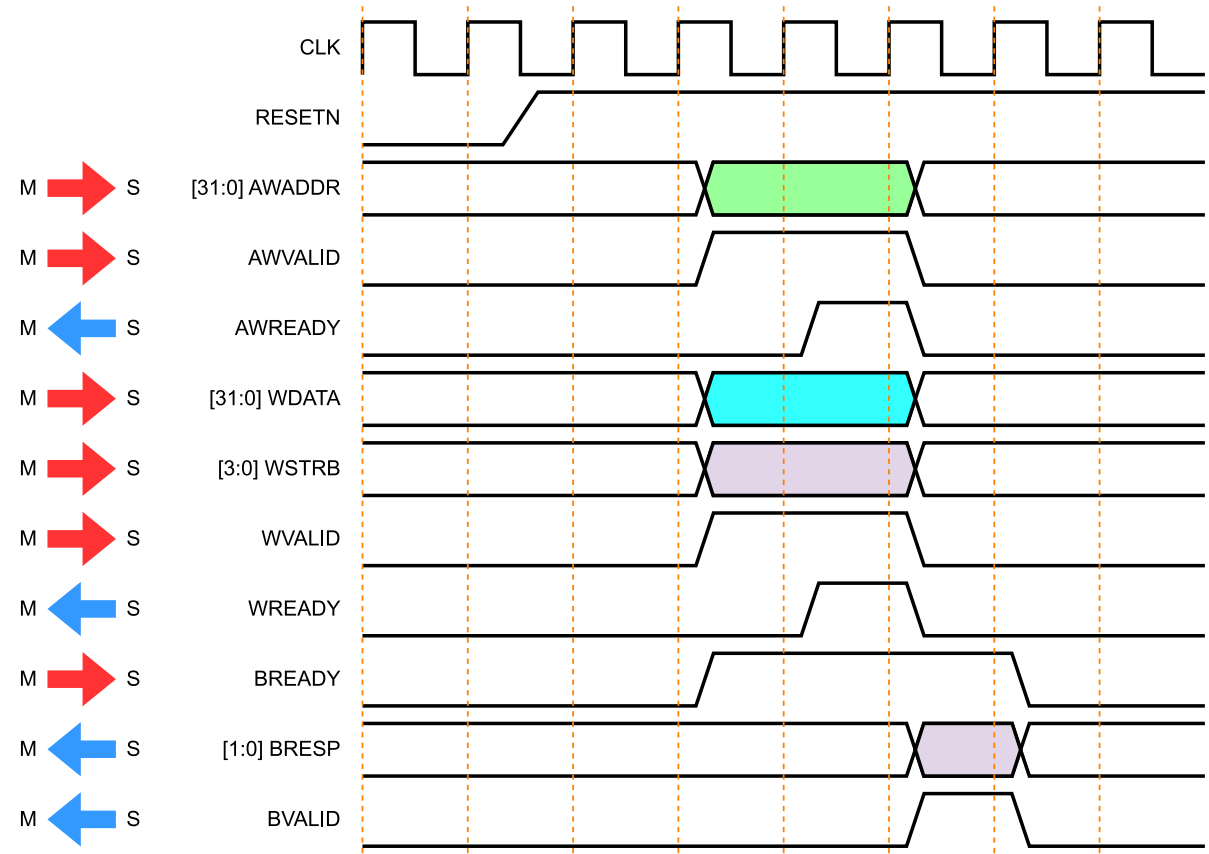

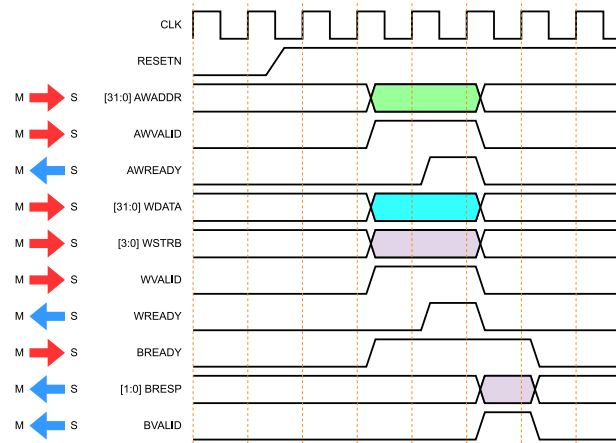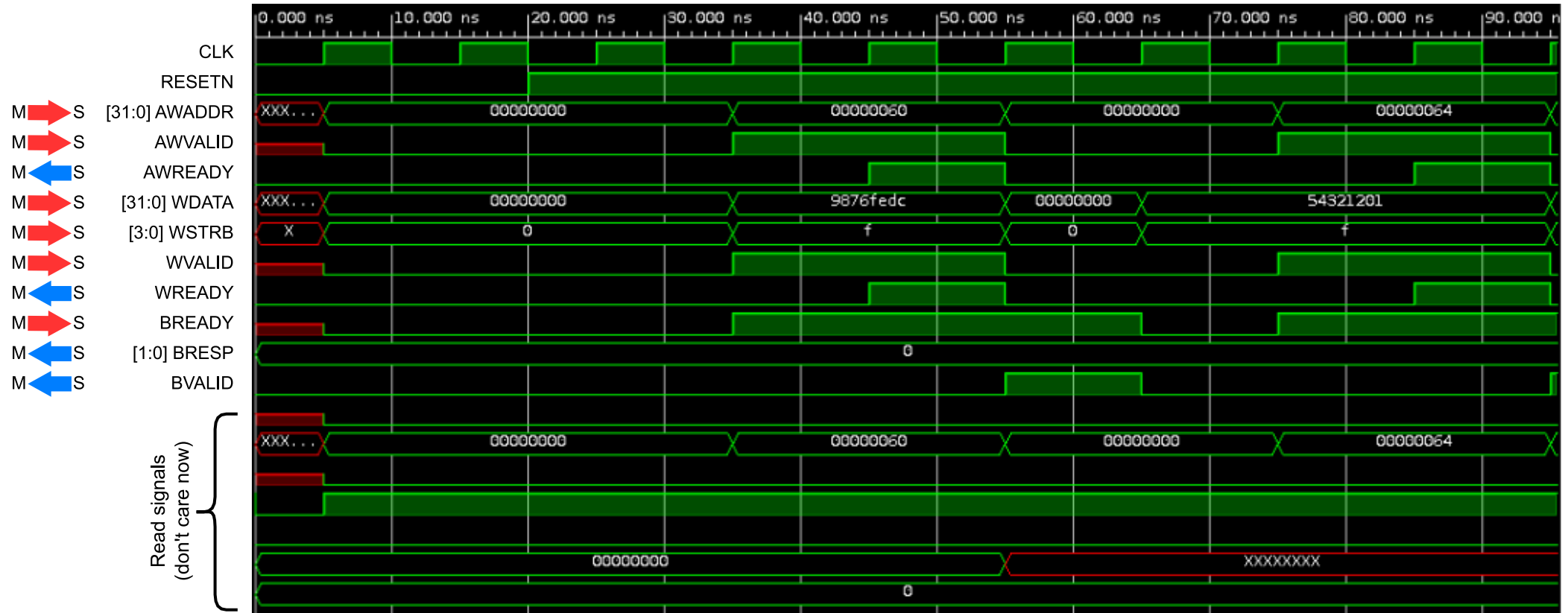Vivado Simulation for AXI4-Lite Write Handshaking




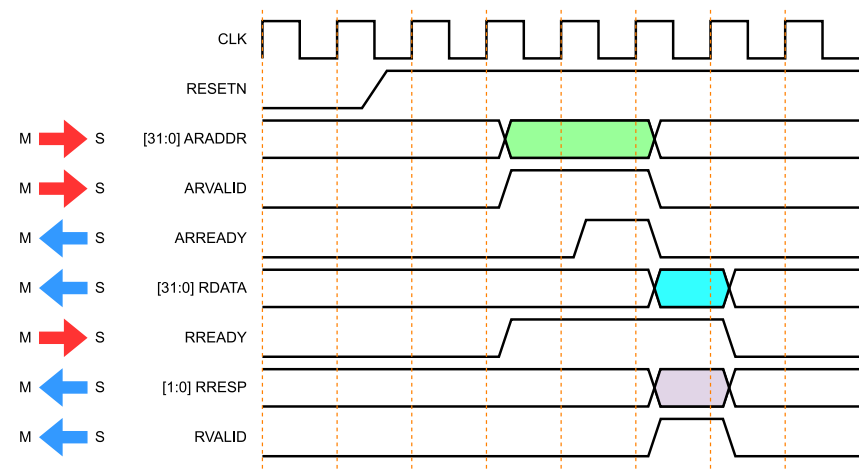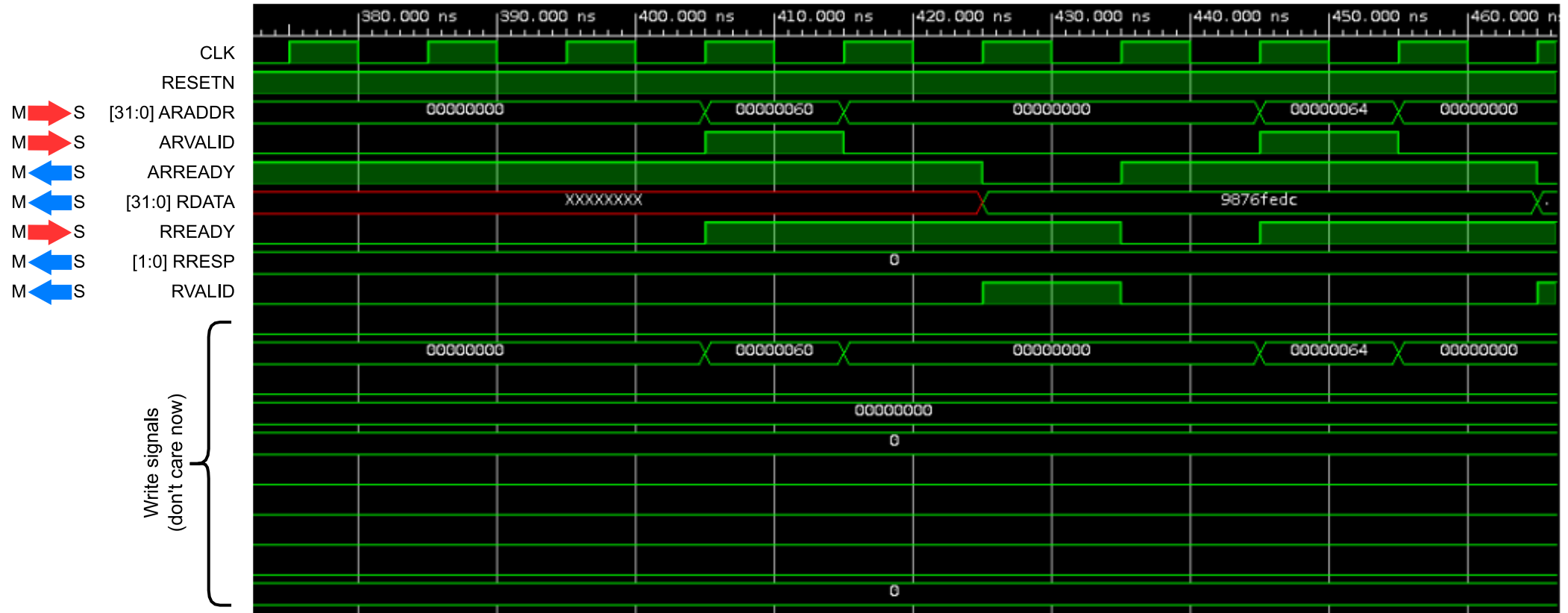Vivado Simulation for AXI4-Lite Read Handshaking




Crossbar Switch

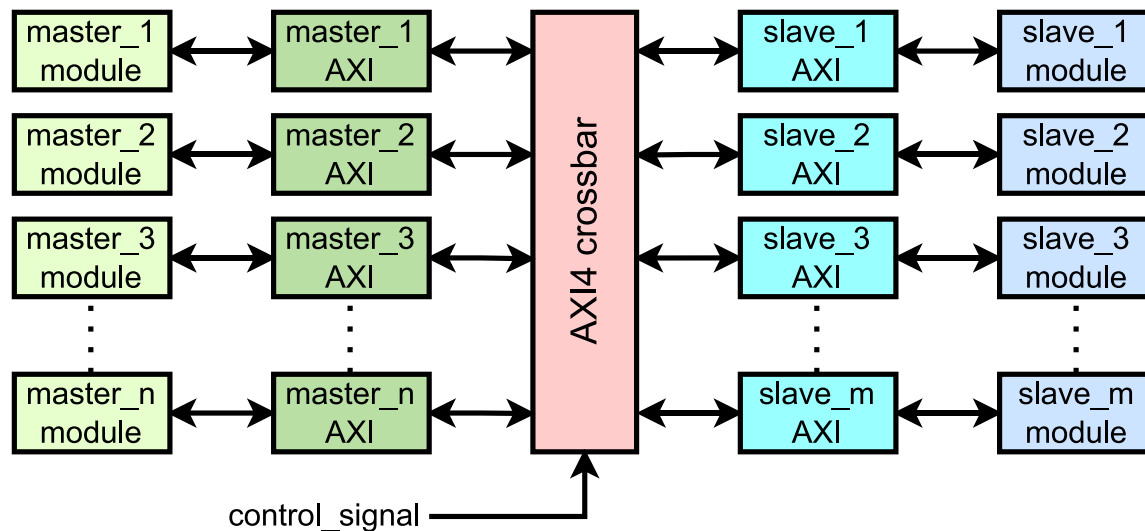
- ✓ Needed when there are multiple masters or multiple slaves.



This project

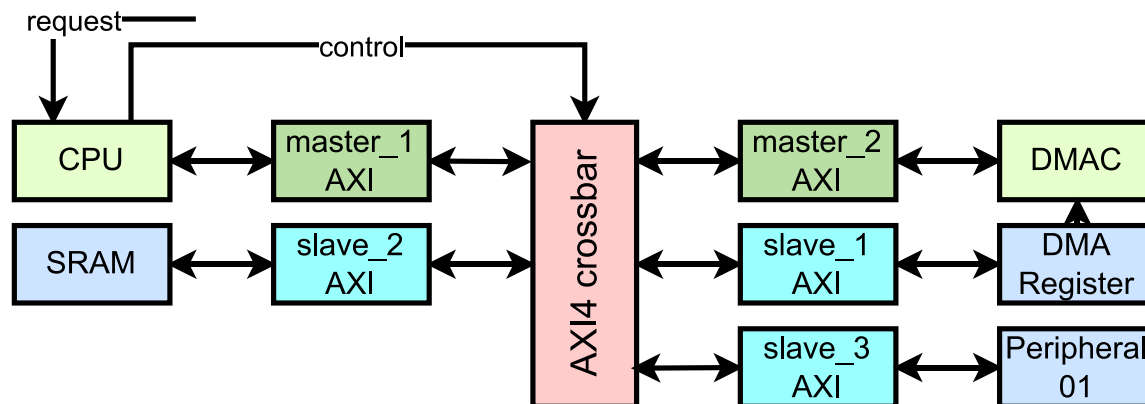


Interrupt Service Routine (ISR)

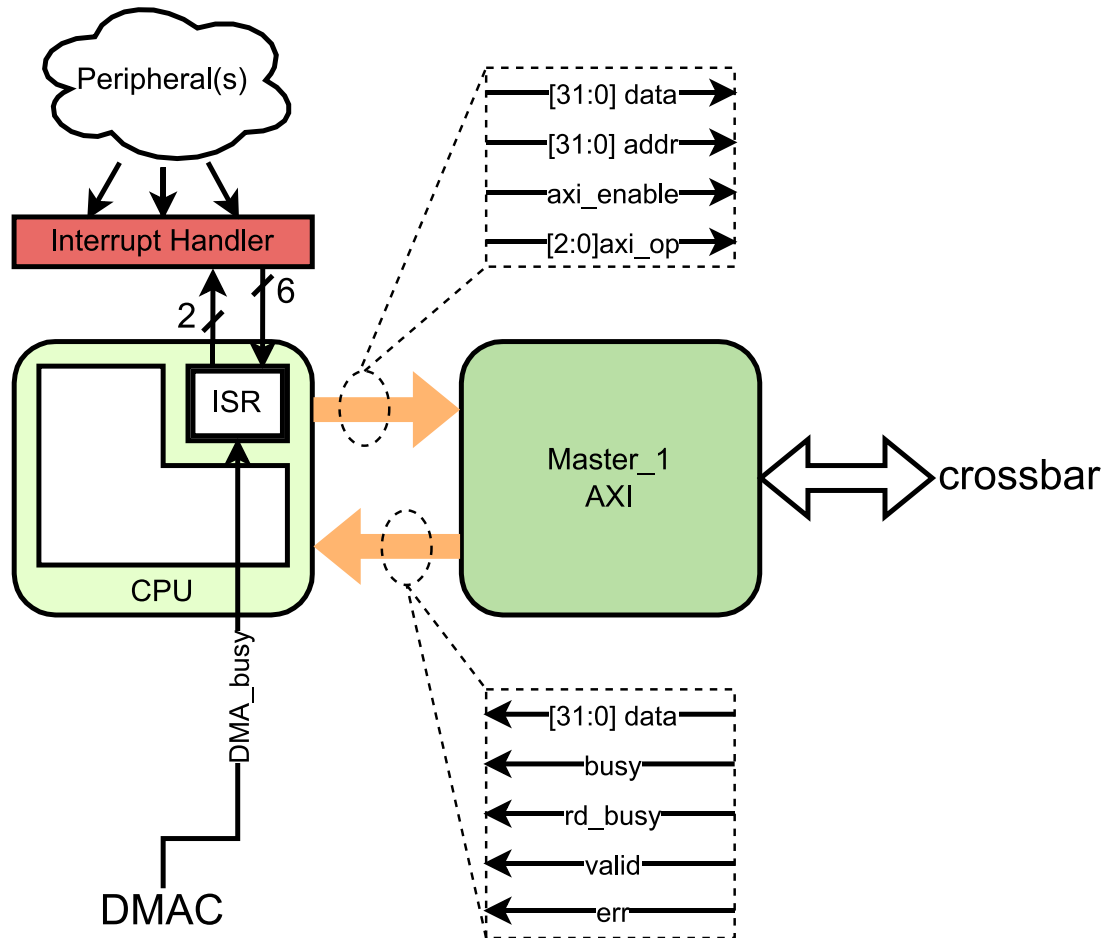

Part of the CPU

- Receives 6-bit service request from the **Interrupt Handler**
- Sends 2-bit status to the **Interrupt Handler**
- Gets DMA status directly from the **DMAC**
- Sends data and address to the **DMA Register** module when suitable
- Controls the **crossbar**

continued (ISR) ...

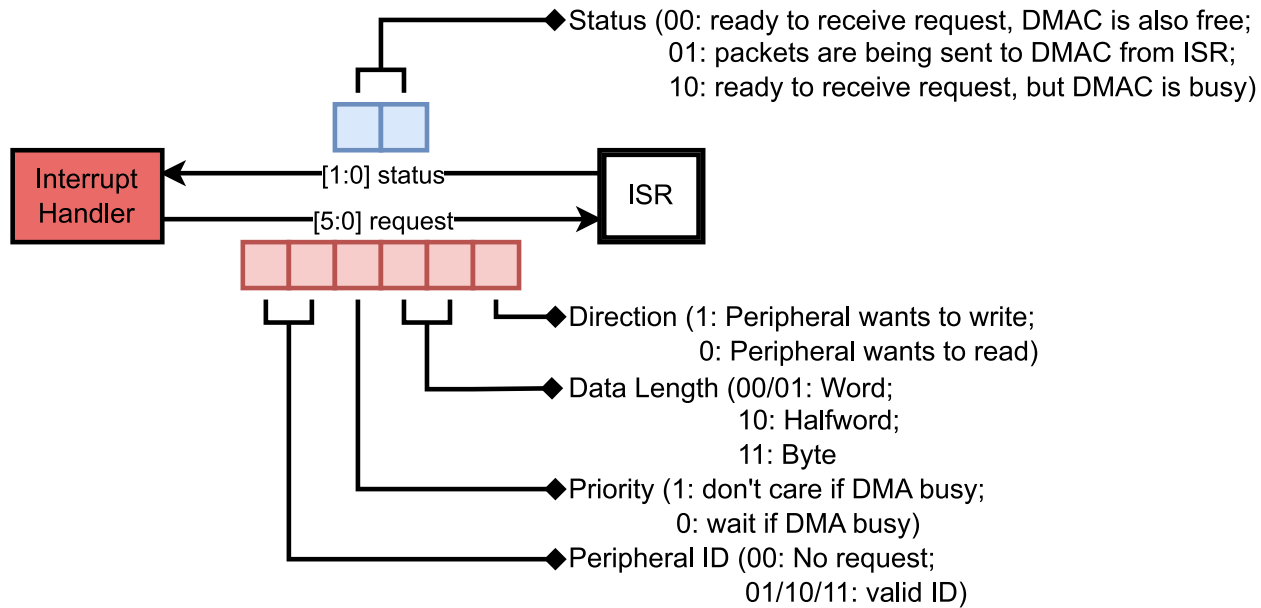

Three packets to be sent to **DMAC** (via **DMA Reg**) from **ISR**:

- **mode**: encapsulates the 6-bit request from the **Interrupt Handler**
- **init_addr**: the starting address of the **SRAM** available for the **DMAC** to read or write
- **range**: how many transaction the **DMAC** would do with the **SRAM**

With appropriate **request**, the **ISR**:

Turns on the **Master1_AXI**


Sends 32-bit **mode** at address $0x000_ABCD$

Sends 32-bit **init_addr** at address $0x000_ABCD + 1$

Sends 32-bit **range** at address $0x000_ABCD + 2$

Turns off the **Master1_AXI**

continued (ISR) ...

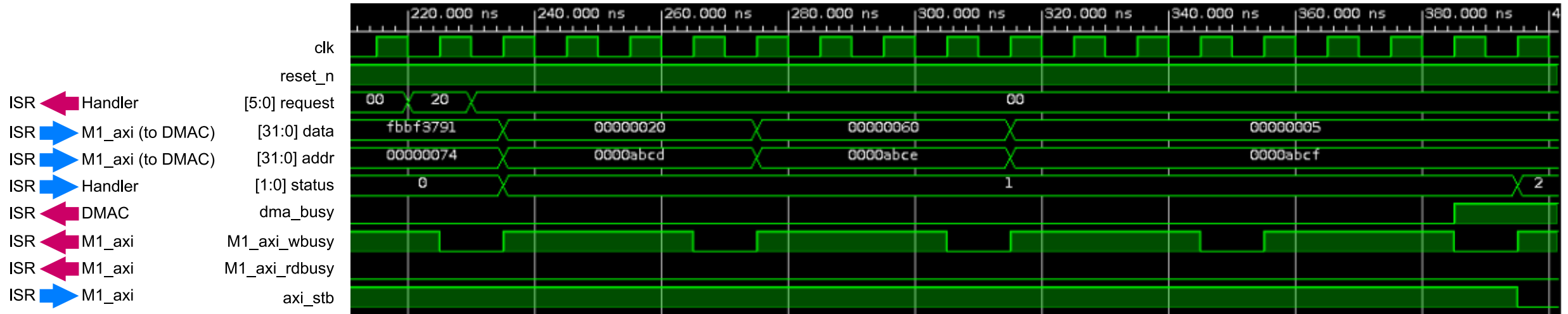

220 New **request** is coming from ID: 2 ('b10_0000) via Handler.

225 Latch the **request**.
M1_AXI is free to write.
Prepare to load **data** and **addr** at next posedge **clk**.


235 Load **mode** into **data**.
Load 0x0000_ABCD into **addr**.
Send **status** as 'b01.
Wait until M1_AXI is free to write.

275 Load **init_addr** into **data**.
Load 0x0000_ABCD+1 into **addr**.
Wait until M1_AXI is free to write.

315 Load **range** into **data**.
Load 0x0000_ABCD+2 into **addr**.



385 DMAC is now busy.
Send **status** as 'b10 to Interrupt Handler at next posedge **clk**.
Stop accessing M1_AXI at next posedge **clk**.

DMA Register

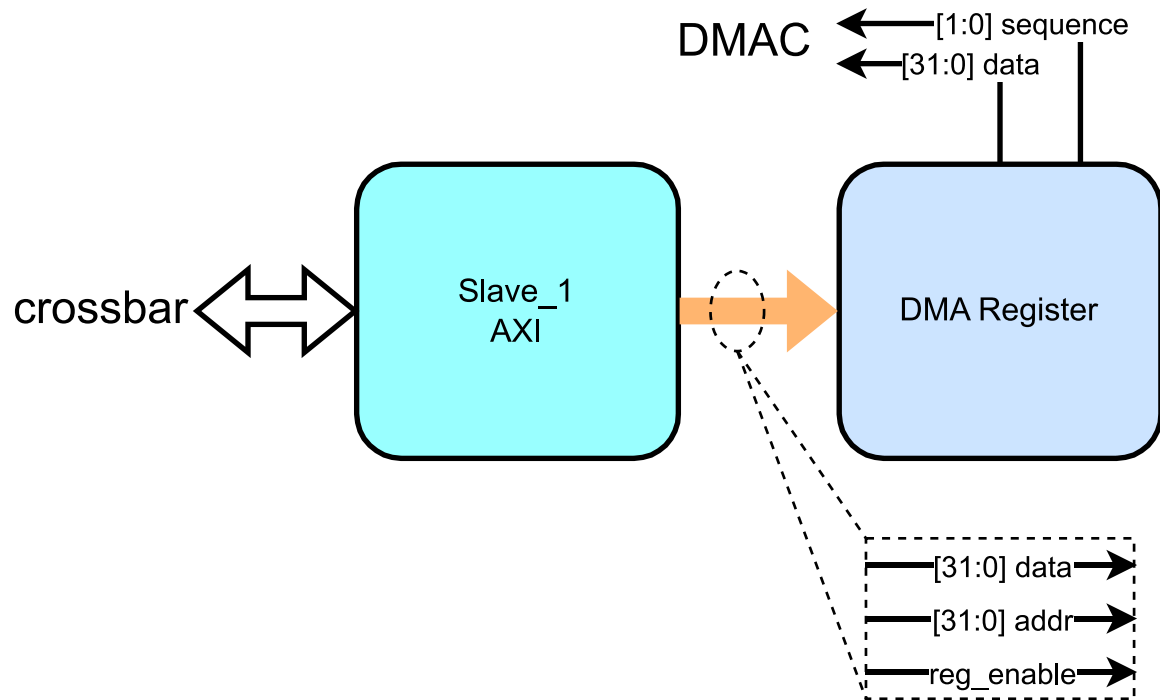


- Verifies the address ($0x0000_ABCD$) from **ISR**
- Transfers **mode**, **init_addr**, **range** packets from **ISR** to **DMAC**
- Sends 2-bit **sequence** info to **DMAC** for discerning those three 32-bit packets

continued (DMA Reg) ...

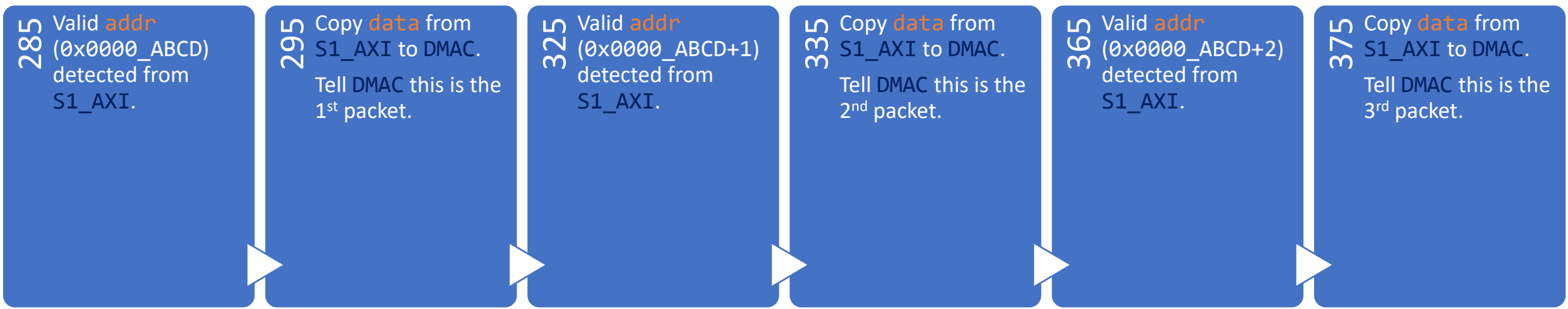
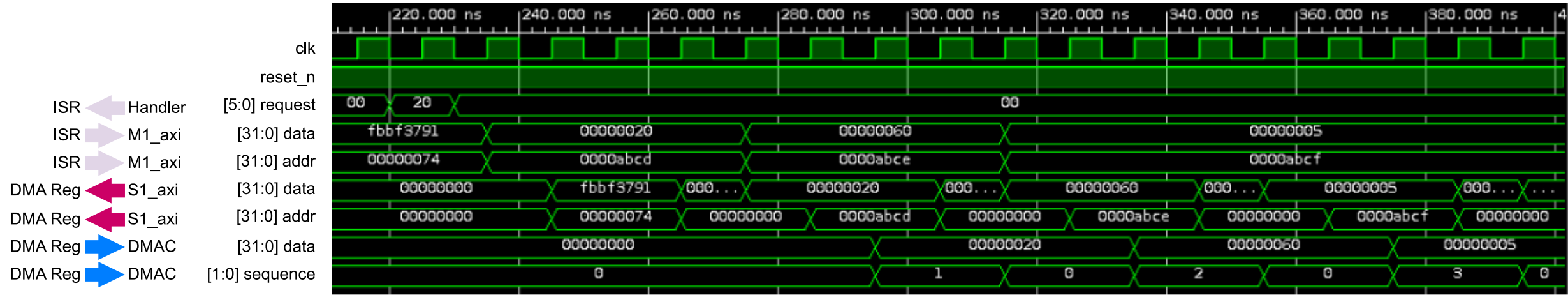


DMAC

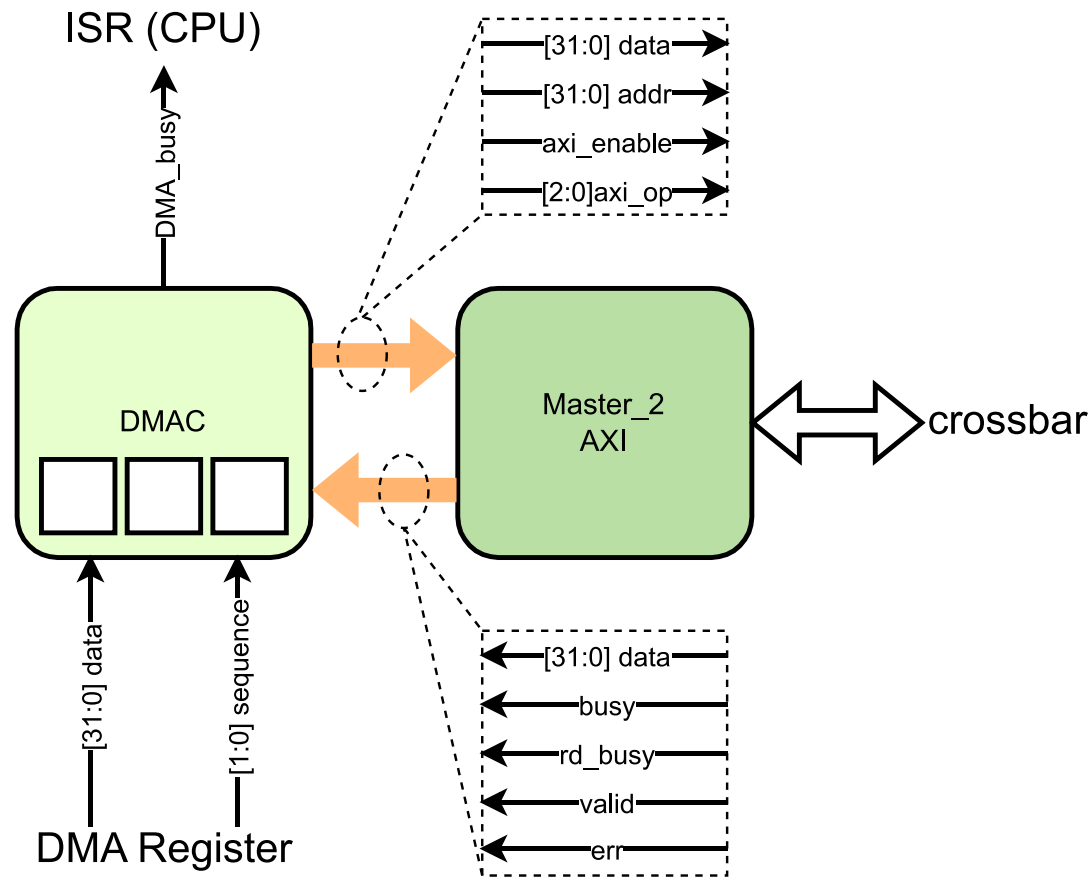


- Has 3 registers to save **mode**, **init_addr**, **range** packets from **DMA Register** module
- Starts transacting with **SRAM** after saving all three packets
- Keeps **DMA_busy** HIGH during transaction with **SRAM**
- Continuously polls if the priority bit (within **mode**) is HIGH

continued (DMAC) ...

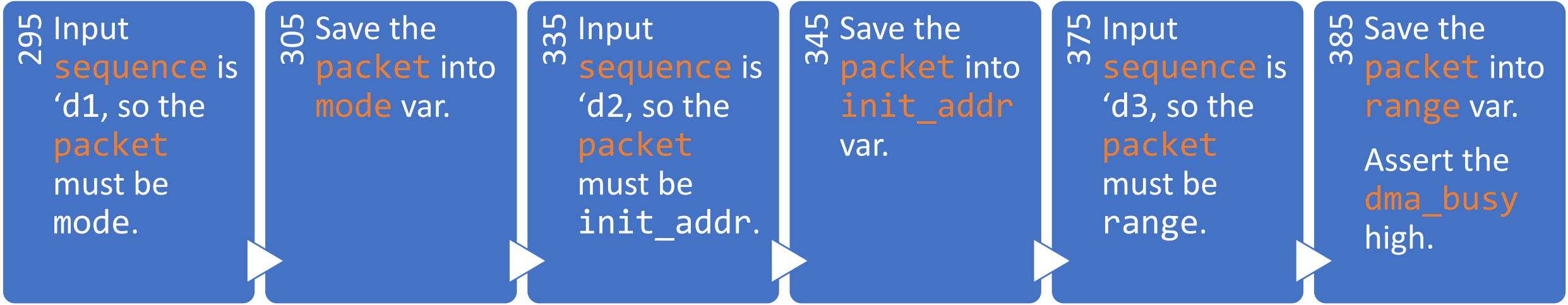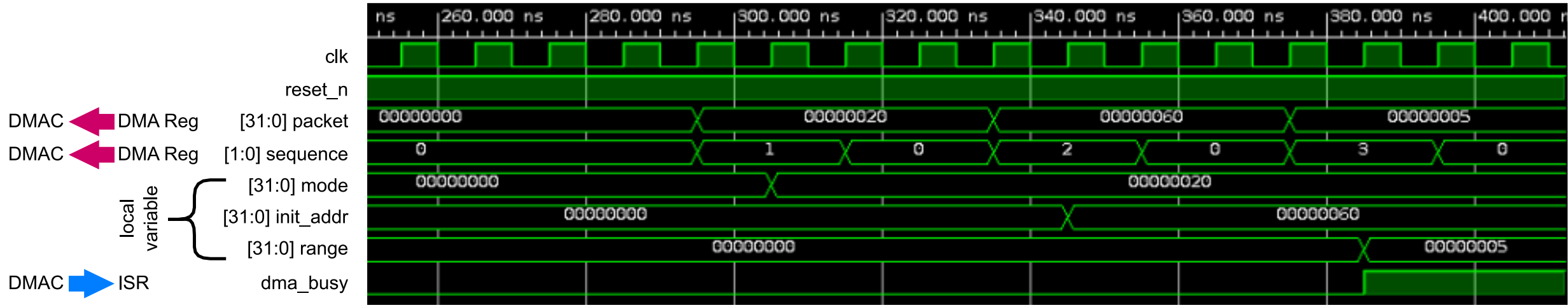

continued (DMAC) ...

 

385 DMAC is ready to access SRAM. Output **dma_busy** is high. M2_AXI is free to read. Load **addr** $0x0000_0060$ at next posedge **clk**.

395 M2_AXI is free to read. Load **addr** $0x0000_0060+(4)$ at next posedge **clk**.


435 M2_AXI is free to read. Load **addr** $0x0000_0060+(4 \times 2)$ at next posedge **clk**.

475, 515, 555 Repeat for **addr** $0x0000_0060+(4 \times 3)$, $0x0000_0060+(4 \times 4)$, $0x0000_0060+(4 \times 5)$

595 M2_AXI is free to read. But **range** is exhausted. Assert the **dma_busy** low at next posedge **clk**. Stop accessing M2_AXI at next posedge **clk**.

But why increment by 4 (instead of 1)?


SRAM Wrapper

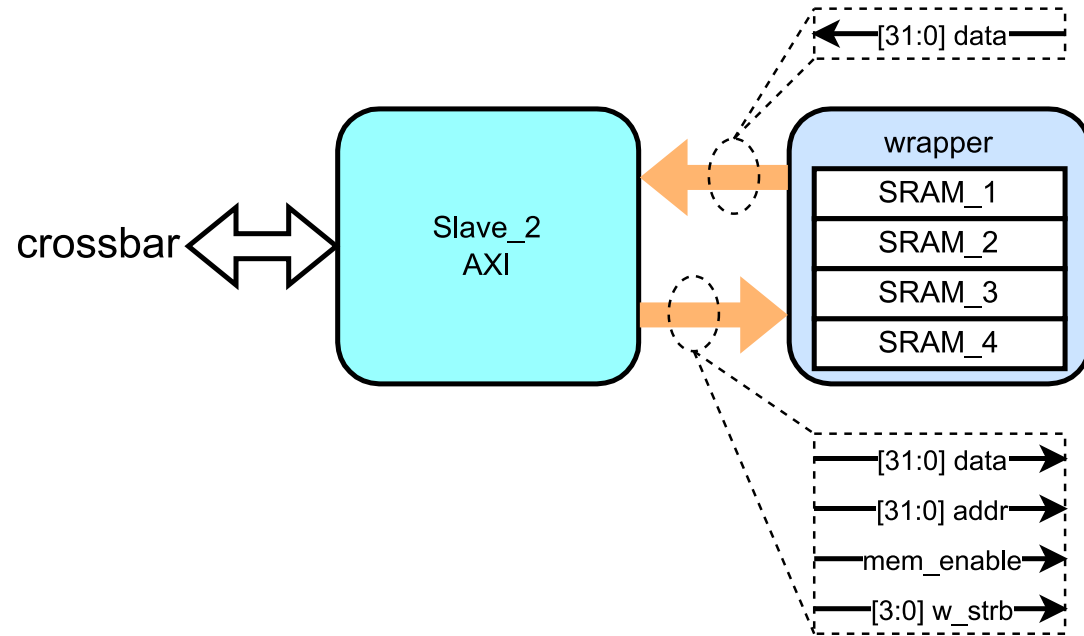

- Encapsulates 4 banks of **SRAM** block, each sized 16×32×8


Overall Hierarchy

- test (tb_dma_ctrl.sv) (1)
 - DMAC : top_RTL (top_RTL.sv) (5)
 - dummyP : axi_wrap_proc (axi_wrap_proc.sv) (2)
 - ISR : dummyProcessor (dummyProcessor.sv)
 - master : axi_master (axi_master.sv)
 - dmaC : axi_wrap_dma (axi_wrap_dma.sv) (2)
 - dmaControl : dma_ctrl (dma_ctrl.sv)
 - master : axi_master (axi_master.sv)
 - dmaREG : axi_wrap_dmareg (axi_wrap_dmareg.sv) (2)
 - slave : axi_slave (axi_slave.sv)
 - dmaReg : dma_reg (dma_reg.sv)
 - SRAM : axi_wrap_mem (axi_wrap_mem.sv) (2)
 - slave : axi_slave (axi_slave.sv)
 - sharedmem : mem_interface_dmem (mem_interfac
 - genblk1[0].dcell : sram_compiled_array (sram_
 - genblk1[1].dcell : sram_compiled_array (sram_
 - genblk1[2].dcell : sram_compiled_array (sram_
 - genblk1[3].dcell : sram_compiled_array (sram_
 - xbarCentral : crossbar (crossbar.sv)

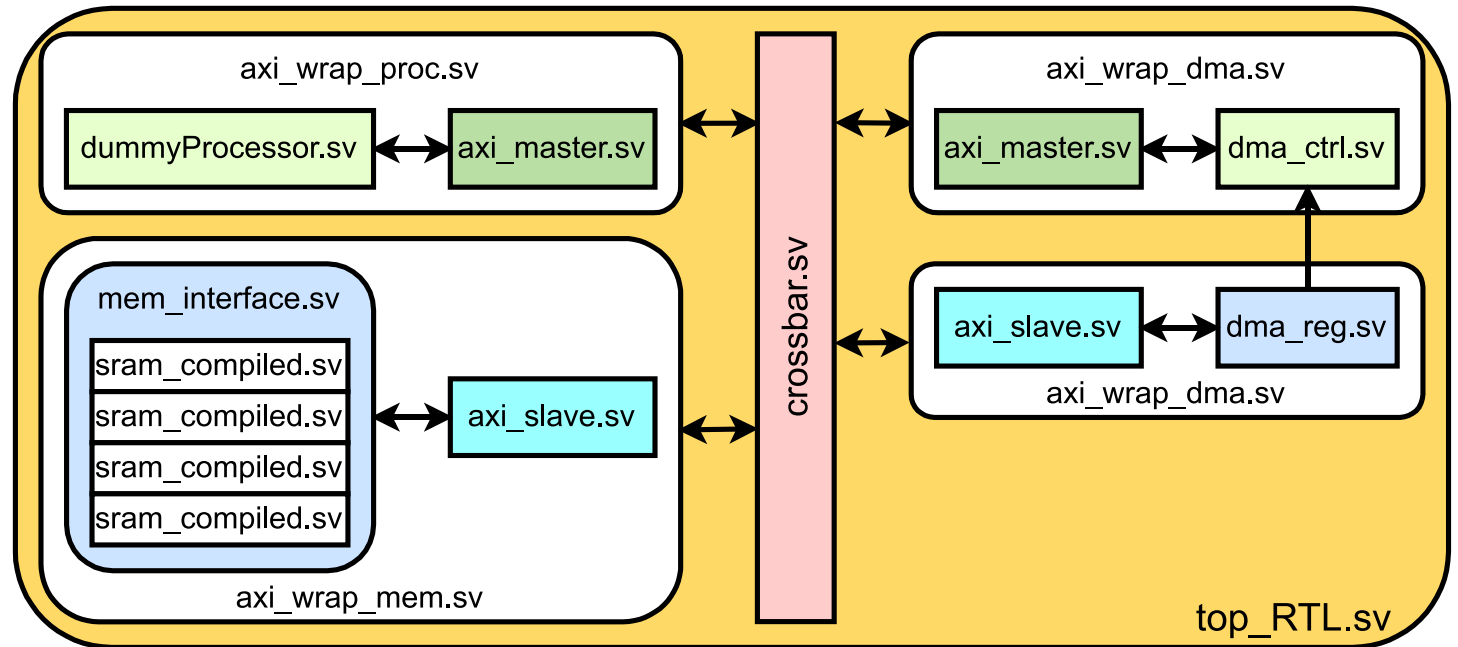


SRAM Transactions

CPU writes to SRAM

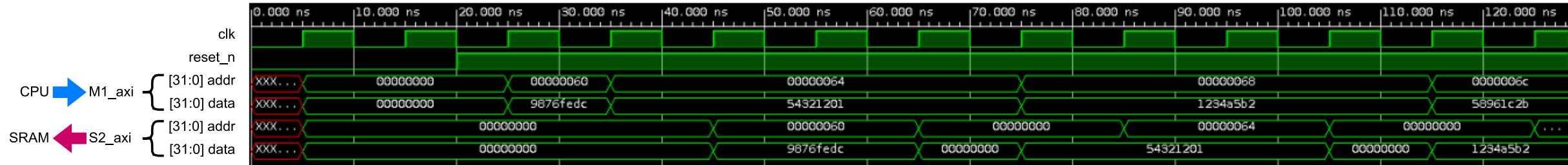

DMAC reads from SRAM

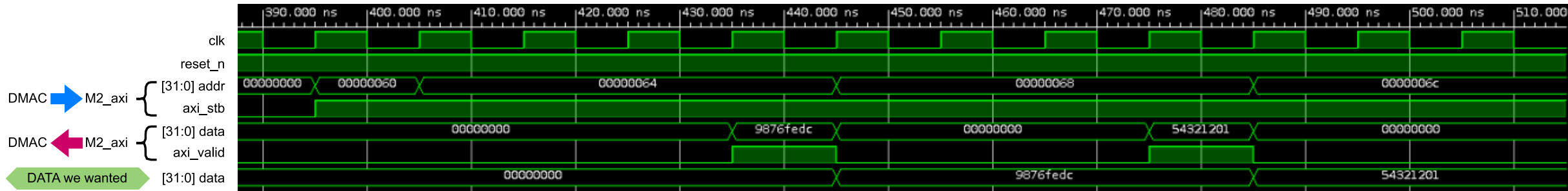

Upcoming Plans

- Add cycle-stealing mode
 - We've only introduced burst mode.
- Attach three dummy peripherals
 - with the Interrupt Handler
- Complete the physical layout
 - with partitioning

Questions?
Comments?
Concerns?